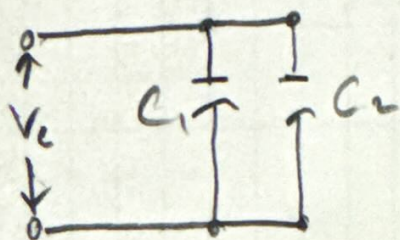


Parallel Case



$$C_1 Q_1 = V_c$$


$$Q_1 = C_1 V_c$$

$$Q_2 = C_2 V_c$$

$$Q = C_1 V_c + C_2 V_c$$

$$Q = (C_1 + C_2) V_c$$

$$C = C_1 + C_2$$

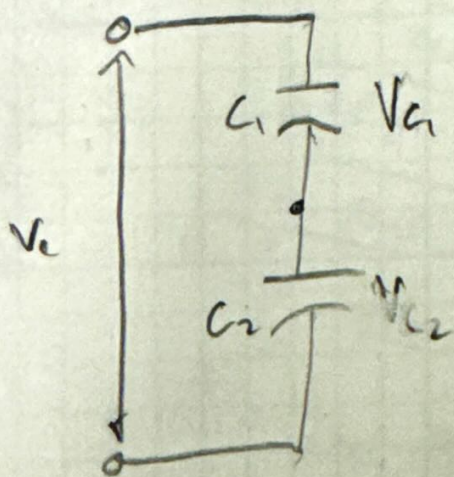Series Case

$$V_c = V_{c1} + V_{c2} \rightarrow Q = Q_1 = Q_2$$

$$\frac{Q}{V_c} = \frac{Q}{C_1} + \frac{Q}{C_2} = Q \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$

The charges of capacitors in series are the same because the same amount of current flows through each capacitor, therefore the amount they are charged is the same.