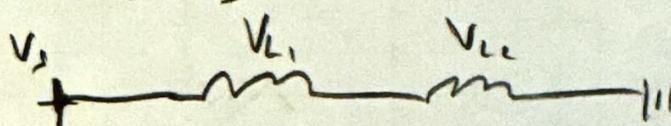


3) Inductance is defined as

$$V_L = L \frac{dI}{dt} \quad L \rightarrow L_{\text{total}}$$

$$V_S = V_{L1} + V_{L2}$$

in series



$$V_S = L_1 \cdot \frac{dI}{dt} + L_2 \cdot \frac{dI}{dt}$$


$$\frac{dI}{dt} L = \frac{dI}{dt} (L_1 + L_2)$$

$\frac{dI}{dt}$ = same for all inductors

→ Same current always running through the leg of the circuit

→ In series
Inductors sum together

parallel case

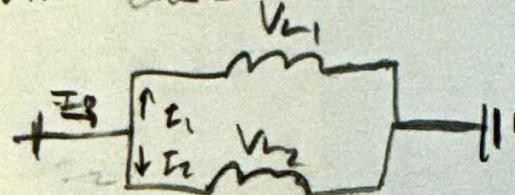

$$\frac{dI_0}{dt} = \frac{dI_1}{dt} + \frac{dI_2}{dt}$$

$$\frac{dI_0}{dt} = \frac{V_S}{L}$$

$$V_S = V_{L1} = L_1 \cdot \frac{dI_1}{dt}$$

$$V_S = V_{L2} = L_2 \cdot \frac{dI_2}{dt}$$

$$\frac{V_S}{L_1} = \frac{dI_1}{dt} \quad \frac{V_S}{L_2} = \frac{dI_2}{dt}$$

$$\rightarrow \frac{dI_0}{dt} = \frac{V_S}{L_2} + \frac{V_S}{L_1}$$

$$\frac{1}{L} = \frac{1}{L_2} + \frac{1}{L_1}$$

Inductors in parallel add together Inversely